

浙江大学

本科实验报告

课程名称: 计算机体系结构

姓 名: 王俊

学 院: 海洋学院

专 业: 海洋工程与技术

学 号: 3170100186

指导教师: 翁恺

2020 年 11 月 13 日

Lab4—Pipelined CPU with stall

课程名称: 计算机体系结构

实验类型: 综合

实验项目名称: 用 stall 解决数据冲突

学生姓名: 王俊 专业: 海洋工程与技术 学号: 3170100186

同组学生姓名: None

指导老师: 翁恺

实验地点: 曹光彪西-301

实验日期: 2020 年 11 月 13 日

一、实验目的和要求

Experiment Purpose:

- Understand the principles of Pipelined CPU Stall
- Understand the principles of Data hazard
- Master the method of Pipelined CPU Stalls Detection and Stall the Pipeline.
- master methods of program verification of Pipelined CPU with Stall

Experiment Apparatus:

- Computer (Intel Core i5 or higher, 4GB RAM or higher) system
- Sword-V4 development board
- Xilinx ISE 14.4 and above development tools

Experimental Materials:

No


二、实验内容和原理

2.1.Experimental task:

- Design the Stall Part of Datapath of 5-stages Pipelined CPU
- Modify the CPU Controller, adding Condition Detection of Stall.
- Verify the Pp. CPU with program and observe the execution of program

2.2.Basic principle

2.2.1.Computer system decomposition

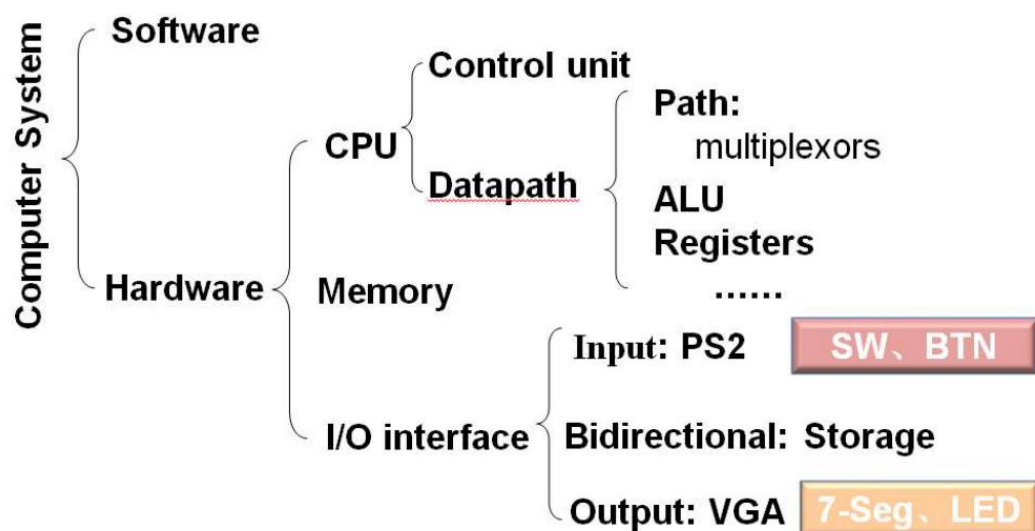


2.2.2.Definition of data hazard:

•**Data Hazards arise when an instruction depends on the results of a previous instruction in a way that is exposed by the overlapping of instructions in the pipeline.**


•When inst. i executes before instr. j, there are data hazards:

- RAW, i.e. instr. j read a source before instr. i writes it.
- WAW, i.e. instr. j write an operand before instr. i writes it.
- WAR, i.e. instr. j write a destination before instr. i read it.


Instruction demo:

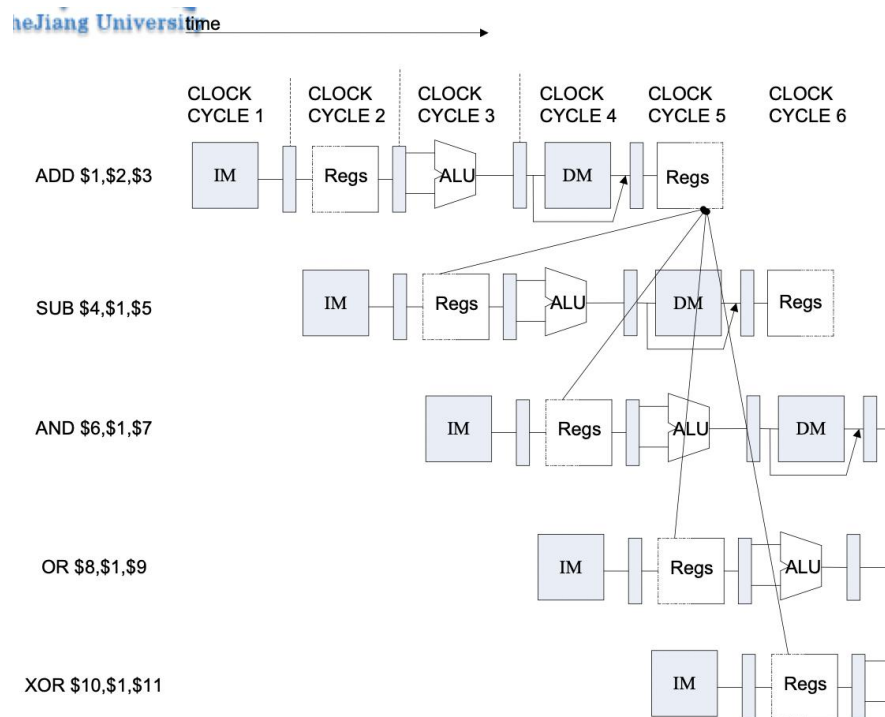

Data Hazard Causes Stalls:

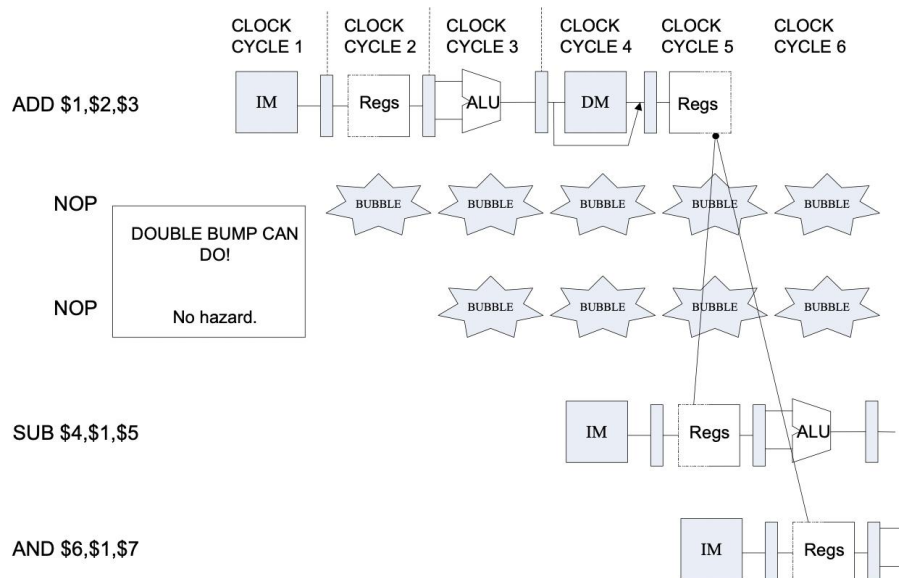


And how to Stall the Pipeline?

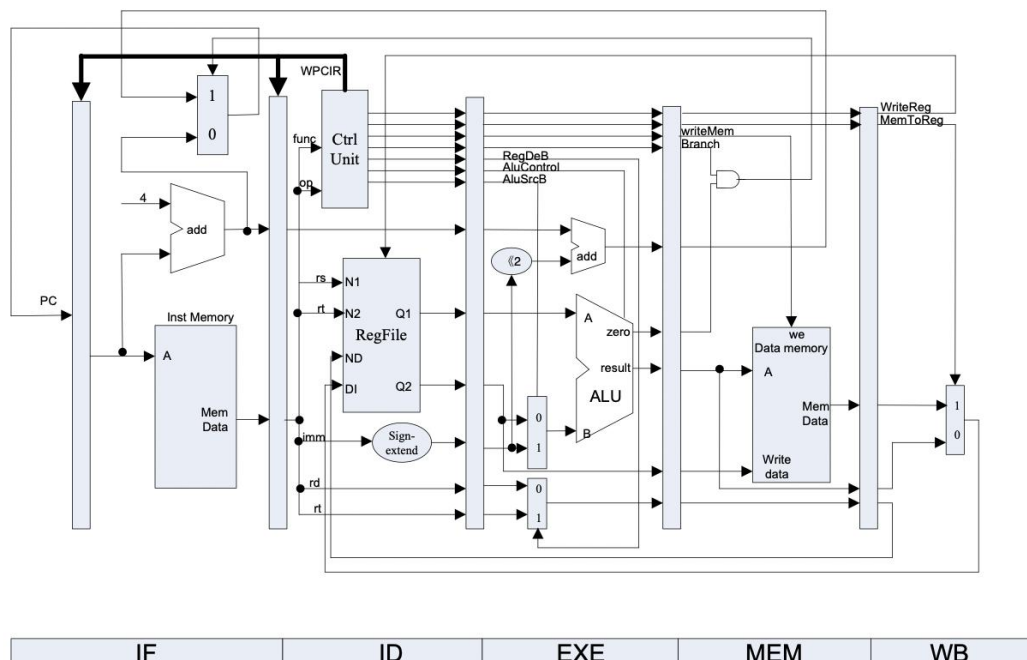


2.2.3.Datapath of 5-stages pipelined CPU

- The datapath from the slides:

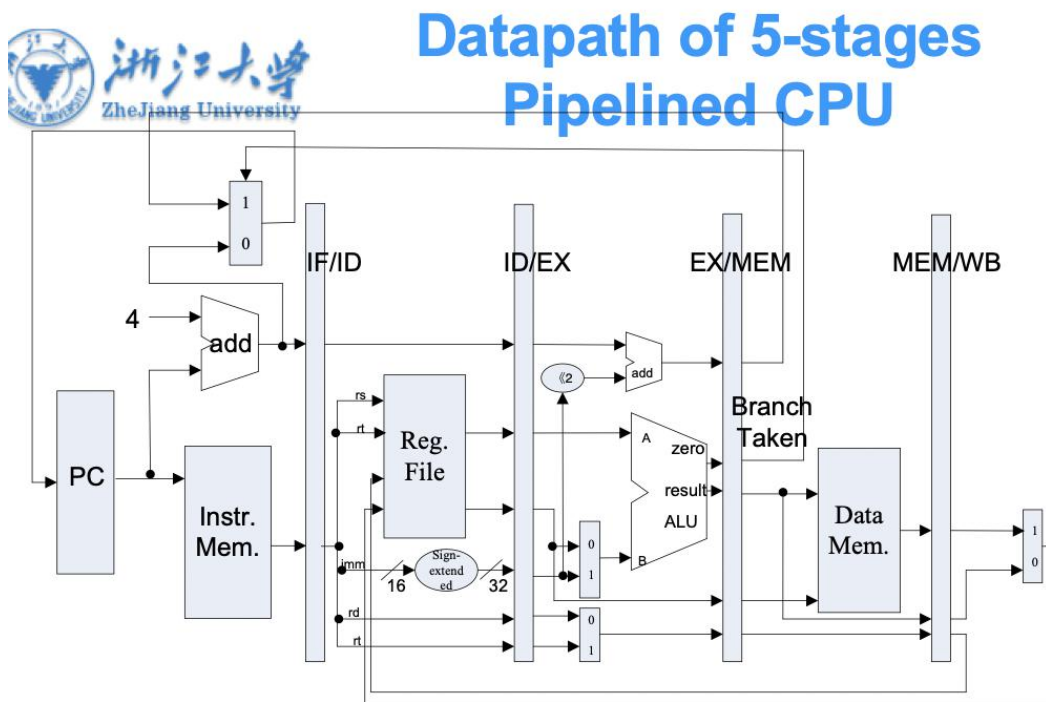

- My design:

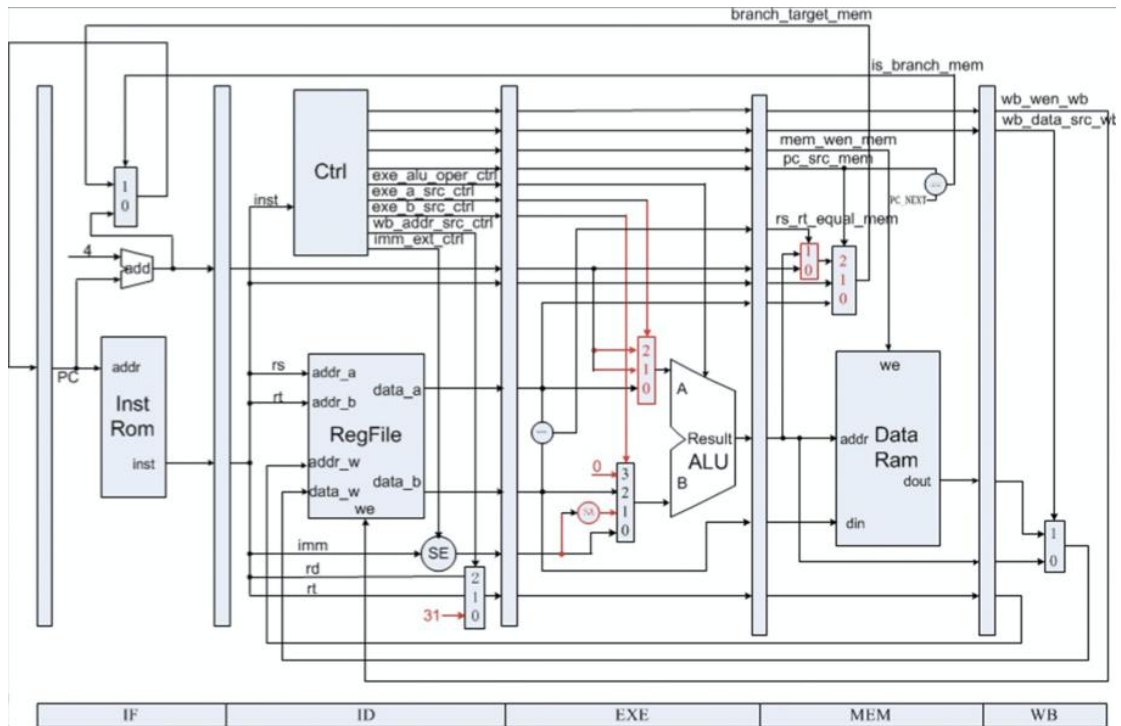

三、实验过程

3.1.Add rt-used and rs-used in the instructions:

```

case (inst[31:26])
  INST_R: begin
    case (inst[5:0])
      R_FUNC_JR: begin
        pc_src = PC_JR;
        rs_used = 1;
      end
      R_FUNC_ADD: begin
        exe_alu_oper = EXE_ALU_ADD;
        wb_addr_src = WB_ADDR_RD;
        wb_data_src = WB_DATA_ALU;
        wb_wen = 1;
        rs_used = 1;
        rt_used = 1;
      end
      R_FUNC_SUB: begin
        exe_alu_oper = EXE_ALU_SUB;
        wb_addr_src = WB_ADDR_RD;
        wb_data_src = WB_DATA_ALU;
        wb_wen = 1;
        rs_used = 1;
        rt_used = 1;
      end
      R_FUNC_AND: begin
        exe_alu_oper = EXE_ALU_AND;
        wb_addr_src = WB_ADDR_RD;
        wb_data_src = WB_DATA_ALU;
        wb_wen = 1;
        rs_used = 1;
        rt_used = 1;
      end
      R_FUNC_OR: begin
        exe_alu_oper = EXE_ALU_OR;
        wb_addr_src = WB_ADDR_RD;
        wb_data_src = WB_DATA_ALU;
        wb_wen = 1;
        rs_used = 1;
        rt_used = 1;
      end
      R_FUNC_SLT: begin
        exe_alu_oper = EXE_ALU_SLT;
        wb_addr_src = WB_ADDR_RD;
        wb_data_src = WB_DATA_ALU;
        wb_wen = 1;
        rs_used = 1;
        rt_used = 1;
      end
    end
  end
end

```

```

INST_J: begin
    pc_src = PC_JUMP;
end
INST_JAL: begin
    pc_src = PC_JUMP;
    exe_a_src = EXE_A_LINK;
    exe_b_src = EXE_B_LINK;
    exe_alu_oper = EXE_ALU_ADD;    //PC+4
    wb_addr_src = WB_ADDR_LINK;
    wb_data_src = WB_DATA_ALU;
    wb_wen = 1;
end
INST_BEQ: begin
    pc_src = PC_BEQ;
    exe_a_src = EXE_A_BRANCH;
    exe_b_src = EXE_B_BRANCH;
    exe_alu_oper = EXE_ALU_ADD;
    imm_ext = 1;
    rs_used = 1;
    rt_used = 1;
end
INST_BNE: begin
    pc_src = PC_BNE;
    exe_a_src = EXE_A_BRANCH;
    exe_b_src = EXE_B_BRANCH;
    exe_alu_oper = EXE_ALU_ADD;
    imm_ext = 1;
    rs_used = 1;
    rt_used = 1;
end
INST_ADDI: begin
    imm_ext = 1;
    exe_b_src = EXE_B_IMM;
    exe_alu_oper = EXE_ALU_ADD;
    wb_addr_src = WB_ADDR_RT;
    wb_data_src = WB_DATA_ALU;
    wb_wen = 1;
    rs_used = 1;
end
INST_ANDI: begin
    imm_ext = 1;
    exe_b_src = EXE_B_IMM;
    exe_alu_oper = EXE_ALU_AND;
    wb_addr_src = WB_ADDR_RT;
    wb_data_src = WB_DATA_ALU;
    wb_wen = 1;
    rs_used = 1;
end

```

```

end
INST_ORI: begin
    imm_ext = 0;
    exe_b_src = EXE_B_IMM;
    exe_alu_oper = EXE_ALU_OR;
    wb_addr_src = WB_ADDR_RT;
    wb_data_src = WB_DATA_ALU;
    wb_wen = 1;
    rs_used = 1;
    //?
end
INST_LW: begin
    imm_ext = 1;
    exe_b_src = EXE_B_IMM;
    exe_alu_oper = EXE_ALU_ADD;
    mem_ren = 1;
    wb_addr_src = WB_ADDR_RT;
    wb_data_src = WB_DATA_MEM;
    wb_wen = 1;
    rs_used = 1;
    //?
end
INST_SW: begin
    imm_ext = 1;
    exe_b_src = EXE_B_IMM;
    exe_alu_oper = EXE_ALU_ADD;
    mem_wen = 1;
    rs_used = 1;
    rt_used = 1;
end
default: begin
    unrecognized = 1;
end
endcase
end

```

3.2.To detect data hazard and implement the reg_stall:

- If detect the data hazard, use reg_stall:

Ex For rs:

if rs is needed to be used && the regw_addr is still in the exe and mem stage && there is a write back signal: reg_stall = 1

```
always @(*) begin
    reg_stall = 0;
    if (rs_used && addr_rs != 0) begin
        if (regw_addr_exe == addr_rs && wb_wen_exe) begin
            reg_stall = 1;
        end
        else if (regw_addr_mem == addr_rs && wb_wen_mem) begin
            reg_stall = 1;
        end
    end
    if (rt_used && addr_rt != 0) begin
        if (regw_addr_exe == addr_rt && wb_wen_exe) begin
            reg_stall = 1;
        end
        else if (regw_addr_mem == addr_rt && wb_wen_mem) begin
            reg_stall = 1;
        end
    end
end
end
```

- implement the reg_stall:


this stall indicate that ID is waiting for previous instruction, should insert NOPs between ID and EXE:

```
else if (reg_stall) begin
    if_en = 0;
    id_en = 0;
    exe_rst = 1;
end
```

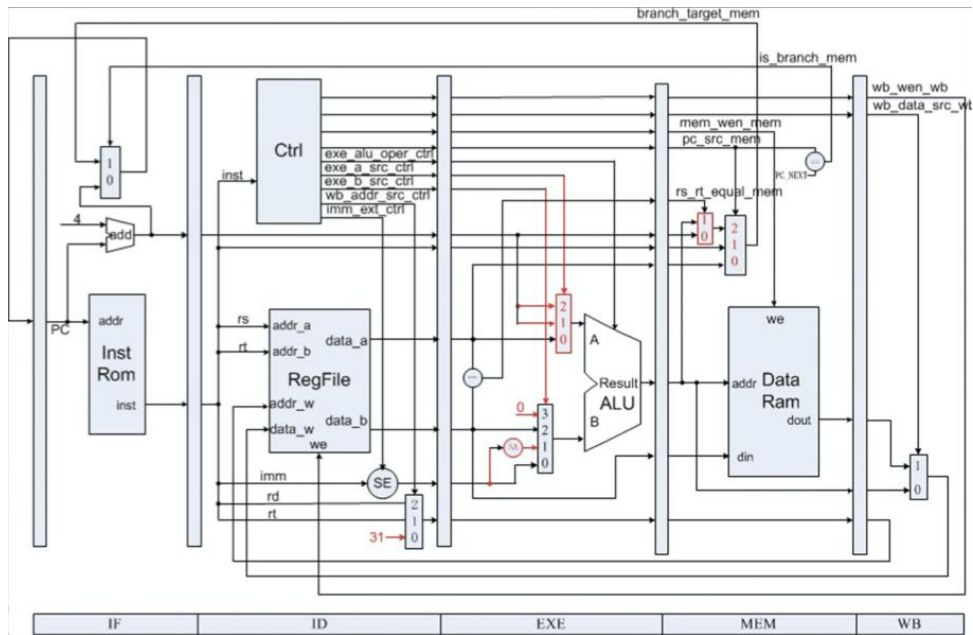3.3.To detect control hazard:

The judge is in the MEM stage:

whether the pc_next is equal to pc_src to decide whether is taken or not?




Condition:

```
always @(*) begin
    branch_stall = 0;
    if (pc_src != PC_NEXT || is_branch_exe || is_branch_mem)
        branch_stall = 1;
end
```

// this stall indicate that a jump/branch instruction is running, so that

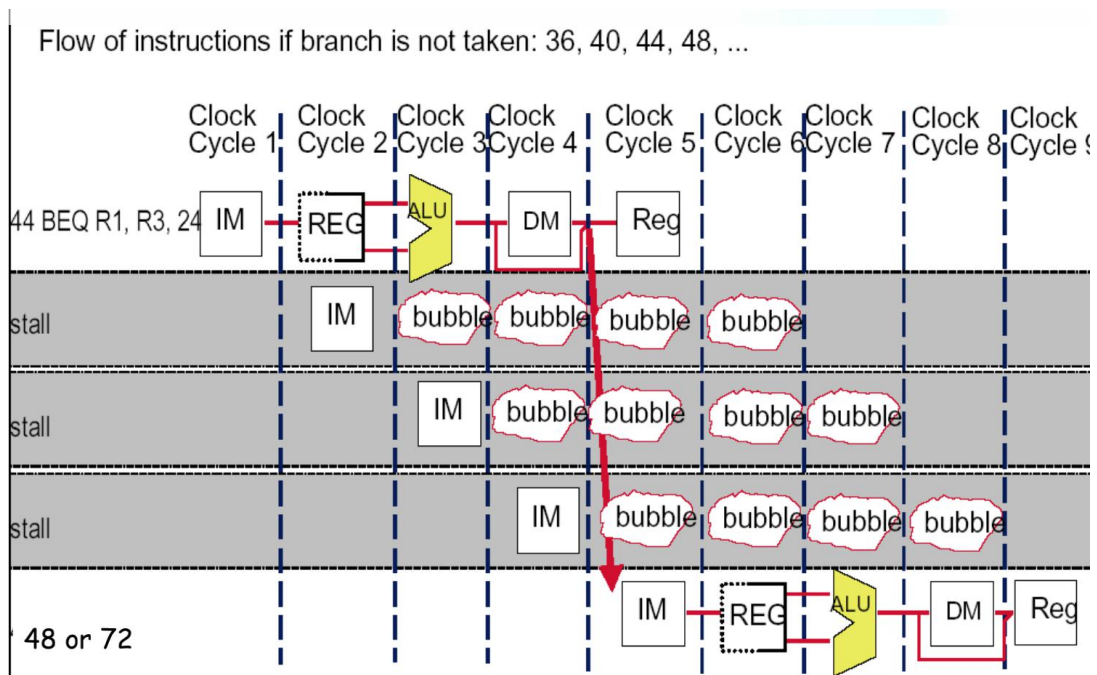3 NOP should be inserted between IF and ID:



Branch-stall:

```
else if (branch_stall) begin
    id_rst = 1;
end
```

Use `pc_src` to judge whether is a branch instruction:

If it is not a branch instruction, `pc_src = pc_NEXT`

```
always @(*) begin
    pc_src = PC_NEXT;
    imm_ext = 0;
    exe_a_src = EXE_A_RS;
    exe_b_src = EXE_B_RT;
    exe_alu_oper = EXE_ALU_ADD;
```

```
INST_BNE: begin
    pc_src = PC_BNE;
    exe_a_src = EXE_A_BRANCH;
    exe_b_src = EXE_B_BRANCH;
    exe_alu_oper = EXE_ALU_ADD
```

To judge whether is a branch instruction in exe and mem stage;

```
always @(*) begin
    is_branch_mem <= (pc_src_mem != PC_NEXT);
end
```

```
always @(*) begin
    is_branch_exe <= (pc_src_exe != PC_NEXT);
end
```

3.4.Each stages:

IF stage with en:

```
// IF stage
assign
    inst_addr_next = inst_addr + 4;

always @(*) begin
    if_valid = ~if_rst & if_en;
    inst_ren = ~if_rst;
end

always @(posedge clk) begin
    if (if_rst) begin
        inst_addr <= 0;
    end
    else if (if_en) begin
        if (is_branch_mem)
            inst_addr <= branch_target_mem;
        else
            inst_addr <= inst_addr_next;
    end
end
```

ID stage with en:

```
// ID stage
always @(posedge clk) begin
    if (id_rst) begin
        id_valid <= 0;
        inst_addr_id <= 0;
        inst_data_id <= 0;
        inst_addr_next_id <= 0;
    end
    else if (id_en) begin
        id_valid <= id_valid;
        inst_addr_id <= inst_addr;
        inst_data_id <= inst_data;
        inst_addr_next_id <= inst_addr_next;
    end
end
```

EXE stage with rst signal:

```
// EXE stage
always @(posedge clk) begin
    if (exe_rst) begin
        exe_valid <= 0;
        inst_addr_exe <= 0;
        inst_data_exe <= 0;
        inst_addr_next_exe <= 0;
        regw_addr_exe <= 0;
        pc_srd_exe <= 0;
        exe_a_src_exe <= 0;
        exe_b_src_exe <= 0;
        data_rs_exe <= 0;
        data_rt_exe <= 0;
        data_imm_exe <= 0;
        exe_alu_oper_exe <= 0;
        mem_ren_exe <= 0;
        mem_wen_exe <= 0;
        wb_data_src_exe <= 0;
        wb_wen_exe <= 0;
    end
    else if (exe_en) begin
        exe_valid <= id_valid;
        inst_addr_exe <= inst_addr_id;
        inst_data_exe <= inst_data_id;
        inst_addr_next_exe <= inst_addr_next_id;
        regw_addr_exe <= regw_addr_id;
        pc_srd_exe <= pc_srd_ctrl;
        exe_a_src_exe <= exe_a_src_ctrl;
        exe_b_src_exe <= exe_b_src_ctrl;
        data_rs_exe <= data_rs;
        data_rt_exe <= data_rt;
        data_imm_exe <= data_imm;
        exe_alu_oper_exe <= exe_alu_oper_ctrl;
        mem_ren_exe <= mem_ren_ctrl;
        mem_wen_exe <= mem_wen_ctrl;
        wb_data_src_exe <= wb_data_src_ctrl;
        wb_wen_exe <= wb_wen_ctrl;
    end
end
```

MEM stage with rst signal:

```

// MEM stage
always @(posedge clk) begin
    if (mem_rst) begin
        mem_valid <= 0;
        pc_src_mem <= 0;
        inst_addr_mem <= 0;
        inst_data_mem <= 0;
        inst_addr_next_mem <= 0;
        regw_addr_mem <= 0;
        data_rs_mem <= 0;
        data_rt_mem <= 0;
        alu_out_mem <= 0;
        mem_ren_mem <= 0;
        mem_wen_mem <= 0;
        wb_data_src_mem <= 0;
        wb_wen_mem <= 0;
        rs_rt_equal_mem <= 0;
    end
    else if (mem_en) begin
        mem_valid <= exe_valid;
        pc_src_mem <= pc_src_exe;
        inst_addr_mem <= inst_addr_exe;
        inst_data_mem <= inst_data_exe;
        inst_addr_next_mem <= inst_addr_next_exe;
        regw_addr_mem <= regw_addr_exe;
        data_rs_mem <= data_rs_exe;
        data_rt_mem <= data_rt_exe;
        alu_out_mem <= alu_out_exe;
        mem_ren_mem <= mem_ren_exe;
        mem_wen_mem <= mem_wen_exe;
        wb_data_src_mem <= wb_data_src_exe;
        wb_wen_mem <= wb_wen_exe;
        rs_rt_equal_mem <= rs_rt_equal_exe;
    end
end
end

```

WB stage:

```

// WB stage
always @(posedge clk) begin
    if (wb_rst) begin
        wb_valid <= 0;
        wb_wen_wb <= 0;
        wb_data_src_wb <= 0;
        regw_addr_wb <= 0;
        alu_out_wb <= 0;
        mem_din_wb <= 0;
    end
    else if (wb_en) begin
        wb_valid <= mem_valid;
        wb_wen_wb <= wb_wen_mem;
        wb_data_src_wb <= wb_data_src_mem;
        regw_addr_wb <= regw_addr_mem;
        alu_out_wb <= alu_out_mem;
        mem_din_wb <= mem_din;
    end
end
end

```

3.5.detail in the bne and beq instruction:

```

assign rs_rt_equal_exe = (data_rs_exe == data_rt_exe); //bne/beq

```


It judge in the mem stage:

```
PC_BEQ: branch_target_mem <= rs_rt_equal_mem ? alu_out_mem : inst_addr_next_mem;
PC_BNE: branch_target_mem <= (!rs_rt_equal_mem) ? alu_out_mem : inst_addr_next_mem;
default: branch_target_mem <= inst_addr_next_mem; // will never used
```

If it is not taken, then `is_branch_mem` will be 0, and a bubble is saved, so it is to predict taken. But it still waste a lot, and I will put the judge in the ID stage in my forwarding job.

四、实验结果分析


编译 bit 文件:

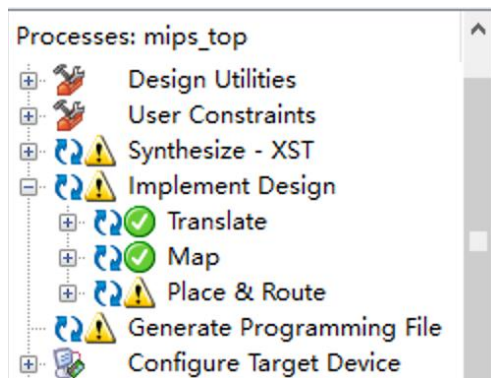


Use the code given:

```
【注释版】
begin:
0    Lw $1, 20($zero)           //R1=4
1    Lw $2, 24($zero)           //R2=1
2    Add $3,$2,$1               //R3=5 //2LW-ALU:forwarding:1 stall
3    Sub $4,$3,$1               //R4=1 //2ALU-ALU
4    And $5,$3,$1               //R5=4 //无冲突
5    Or $6,$3,$1                //R6=5 //无冲突
6    addi $6,$3,4                //$6=9 //无冲突
```

 Put the hex file in the current folder and have a test:



 

Vga:

When it comes to, because there is no forwarding it will insert two bubbles:


```

begin:
0      Lw $1, 20($zero)           //R1=4
1      Lw $2, 24($zero)           //R2=1
2      Add $3,$2,$1                //R3=5 //2LW-ALU:forwarding:1 stall
3      Sub $4,$3,$1               //R4=1 //2ALU-ALU

6      addi $6,$3,4                //$6=9 //无冲突
7      Add $7, $zero, $1           //R7=4 //无冲突
8      Lw $8,0($7)                 //R8=8 //2ALU-LW
9      Sw $8,$8($7)               //      //2LW-SW: forwarding可以解决


```

 And the result is the same as what we predict, so the stall is working!



五、实验总结与反思

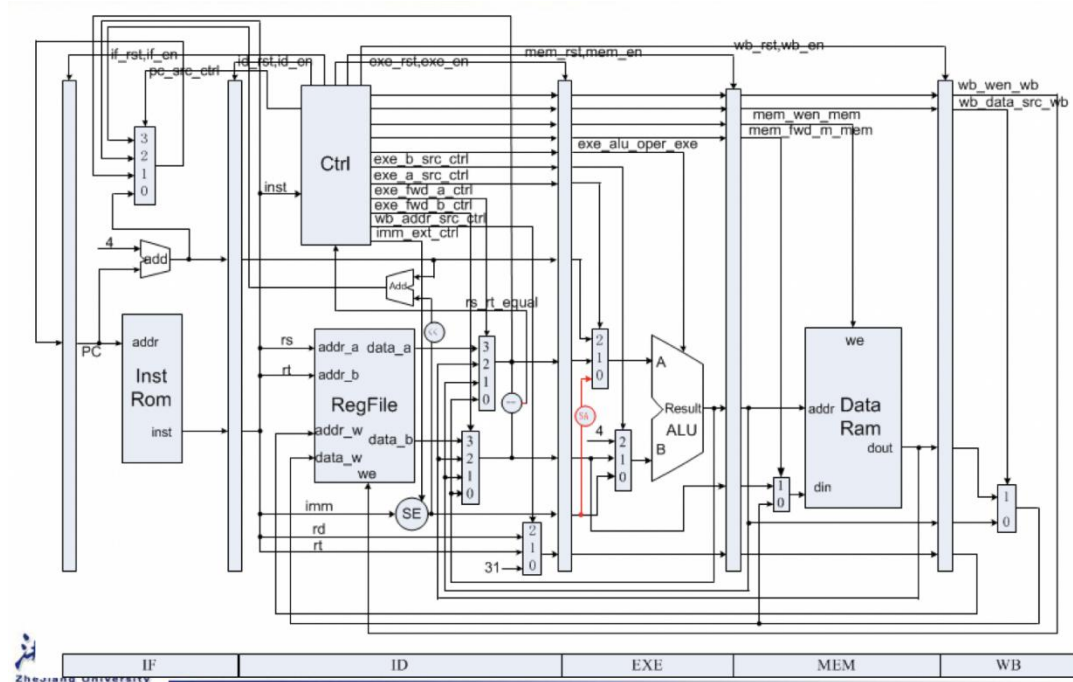1. Specifically, in the implementation of the bne code, the calculation of the address in the EXE stage and the judgment of whether to jump are selected in this stage. In order to facilitate future experiments, the steps of judgment and address calculation should be moved forward. Moreover, in order to advance the ALU module used to calculate the address, an adder should be added as the followings: **so the next one I will use this datapath**



2. The vga debugger is need to be added into every module that has the signals in the following code, and be careful not to miss any:

```
always @(posedge clk) begin
  case (debug_addr[4:0])
    0: debug_data_signal <= inst_addr;
    1: debug_data_signal <= inst_data;
    2: debug_data_signal <= inst_addr_id;
    3: debug_data_signal <= inst_data_id;
    4: debug_data_signal <= inst_addr_exe;
    5: debug_data_signal <= inst_data_exe;
    6: debug_data_signal <= inst_addr_mem;
    7: debug_data_signal <= inst_data_mem;
    8: debug_data_signal <= {27'b0, addr_rs};
    9: debug_data_signal <= data_rs;
    10: debug_data_signal <= {27'b0, addr_rt};
    11: debug_data_signal <= data_rt;
    12: debug_data_signal <= data_imm;
    13: debug_data_signal <= opa_exe;
    14: debug_data_signal <= opb_exe;
    15: debug_data_signal <= alu_out_exe;
    16: debug_data_signal <= 0;
    17: debug_data_signal <= 0;
    18: debug_data_signal <= {19'b0, inst_ren, 7'b0, mem_ren, 3'b0, mem_wen};
    19: debug_data_signal <= mem_addr;
    20: debug_data_signal <= mem_din;
    21: debug_data_signal <= mem_dout;
    22: debug_data_signal <= {27'b0, regw_addr_wb};
    23: debug_data_signal <= regw_data_wb;
    default: debug_data_signal <= 32'hFFFF_FFFF;
  endcase
end
```

For example in the Reg:

```
`ifdef DEBUG
.debug_addr(debug_addr[4:0]),
.debug_data(debug_data_reg),
`endif
```